

ESC102T : Introduction to Electronics

Week3_L14: Transient Analysis of RL Circuits


Adrish Banerjee
Dept. of Electrical Engineering
IIT Kanpur

Acknowledgements

Prof. Baquer Mazhari for the lecture slides

Recall

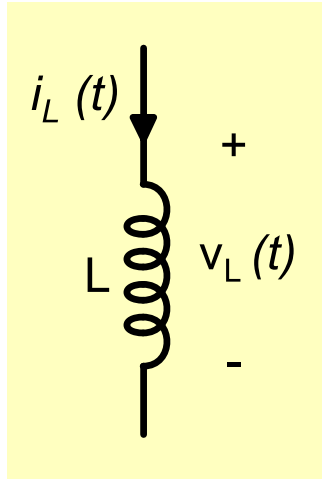Current through an inductor cannot change instantaneously



$$v_L = L \frac{di_L}{dt}$$

$$i_L = \frac{1}{L} \int v_L(t) dt$$

Instant change in voltage implies infinite voltage!

Recall: First Order Differential Equation

$$\frac{dy}{dt} = -a y$$

Solution:


$$y(t) = y(0) e^{-at}$$

$$\frac{dx}{dt} = -a_1 x + a_2$$

Solution:

$$x(t) = x(\infty) + \{x(0) - x(\infty)\} e^{-a_1 t}$$

R-L Transients

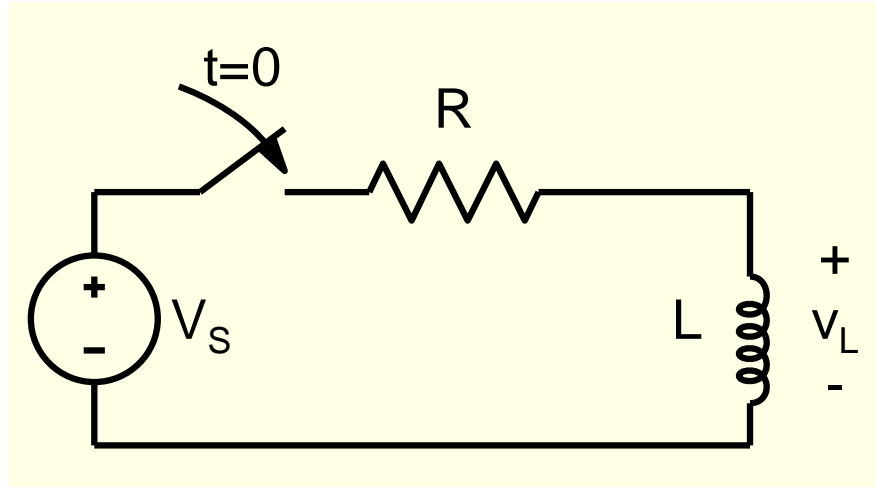

$$v = L \frac{di}{dt}$$

$$Ri(t) + L \frac{di}{dt} = V_s$$

$$\frac{dx}{dt} = -a_1 x + a_2$$

$$x(t) = x(\infty) + \{x(0) - x(\infty)\} e^{-a_1 t}$$


$$i(t) = i(\infty) + \{i(0) - i(\infty)\} e^{-\frac{R}{L}t}$$

$$e^{-\frac{t}{\tau}}$$

$$\text{Time Constant : } \tau = \frac{L}{R}$$

What is $i(\infty)$?

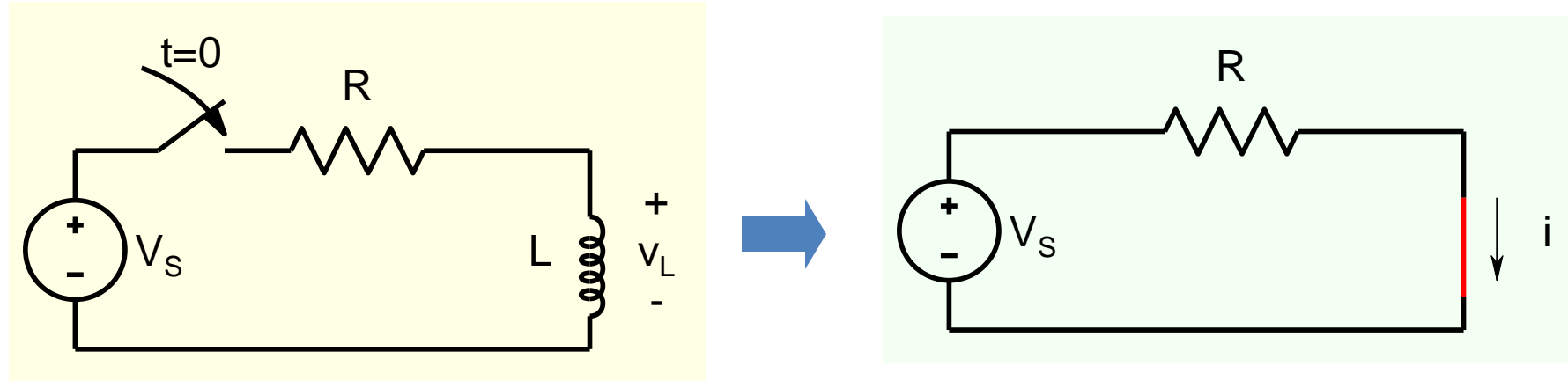Remember that inductor in steady state is like a short circuit




$$i(\infty) = \frac{V_S}{R}$$

$$i(t) = \frac{V_S}{R} + \left\{ i(0) - \frac{V_S}{R} \right\} e^{-\frac{R}{L}t}$$

We also note that inductor current cannot change instantly


Current through an inductor cannot change instantaneously

$$i(0^+) = i(0^-)$$

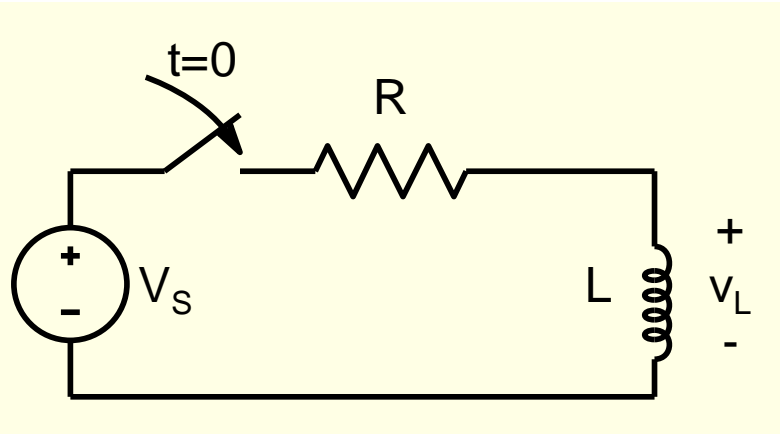


$$i(0^+) = i(0^-) = 0$$
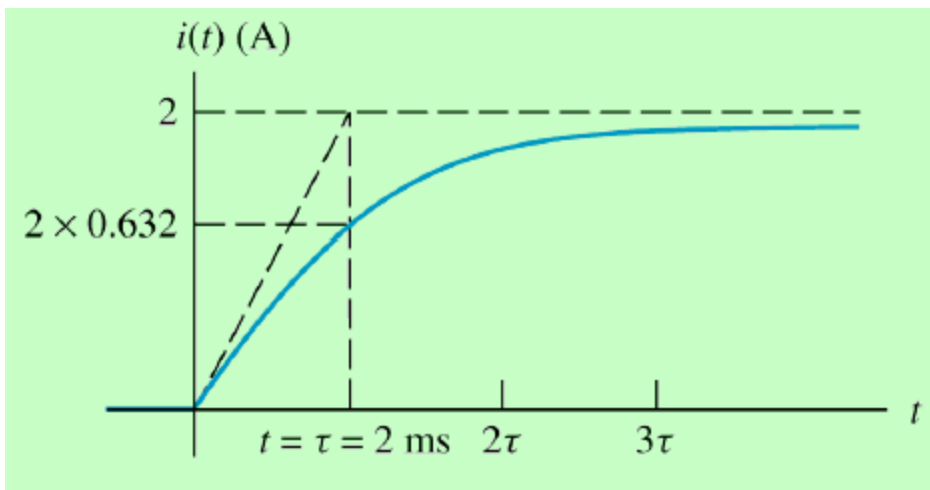
$$i(t) = \frac{V_S}{R} \times (1 - e^{-\frac{t}{\tau}})$$




What about voltage across the Inductor?


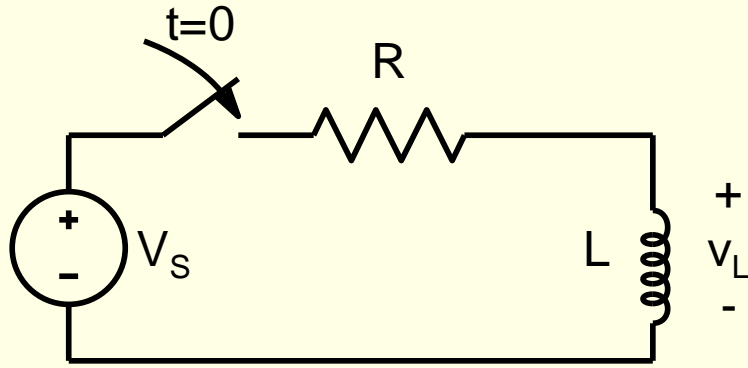


$$i(t) = \frac{V_S}{R} \times (1 - e^{-\frac{t}{\tau}})$$
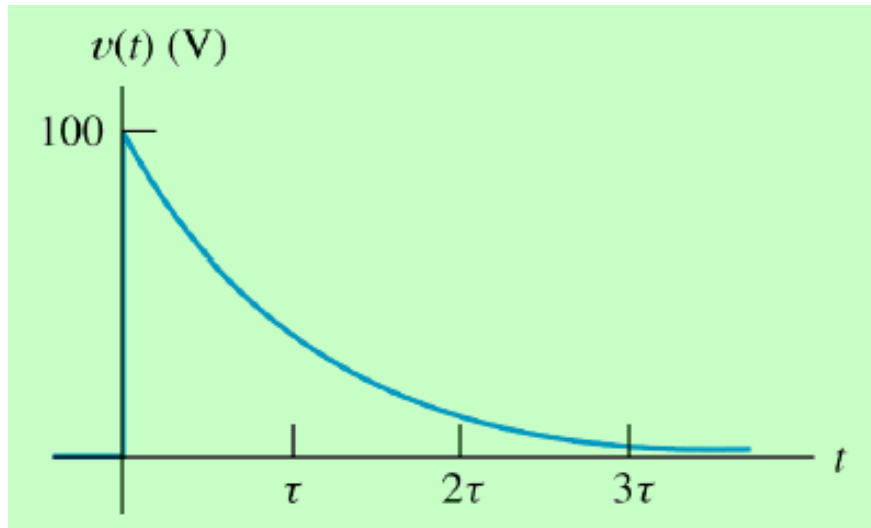
$$v = L \frac{di}{dt} = \frac{L}{R} V_S \times e^{-\frac{t}{\tau}}$$





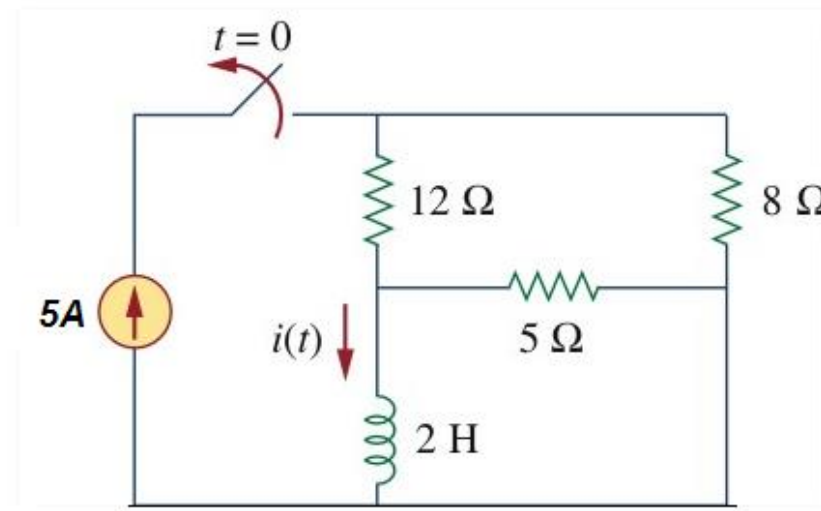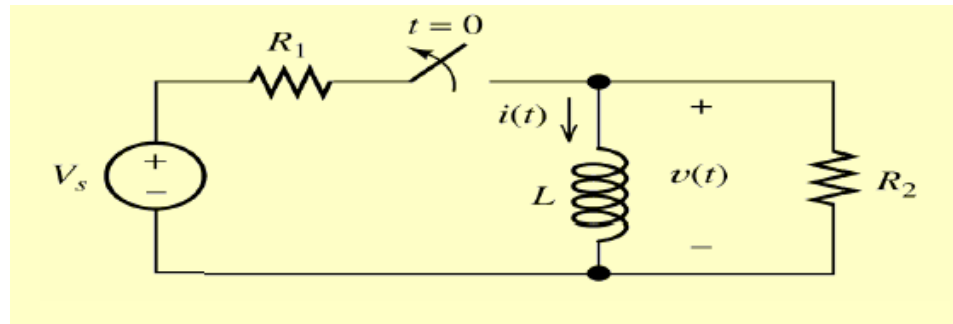How do we solve more complex circuits containing a single inductor?



Method for circuits containing a single inductor

Circuit for $t > 0$

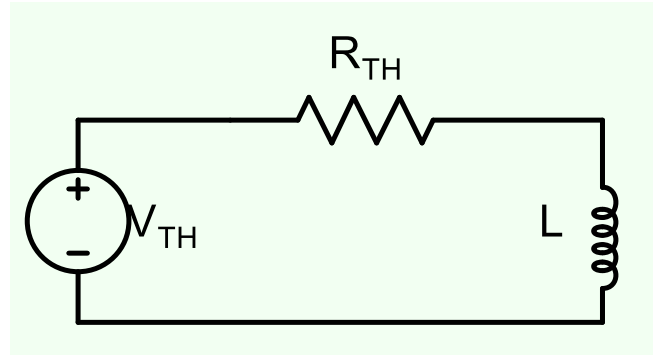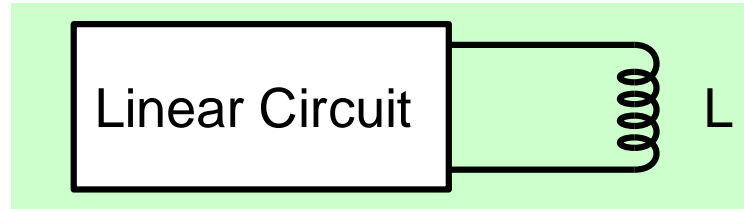


$$x(t) = x(\infty) + \{x(0^+) - x(\infty)\}e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R_{eq}}$$

Where x is inductor current




Example:

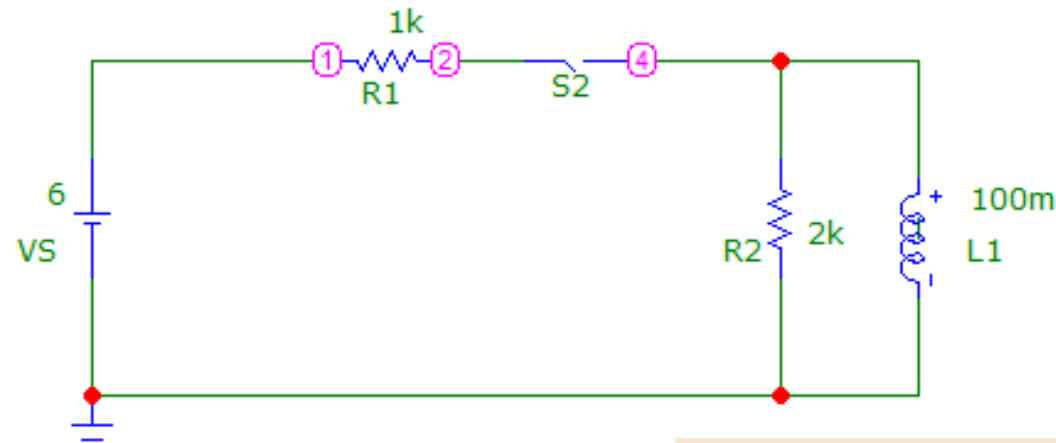

Switch is opened at $t = 0$

Circuit for $t > 0$

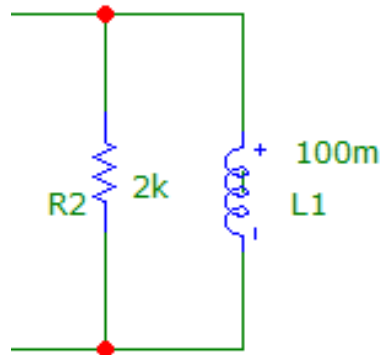

$$i(t) = i(\infty) + \{i(0^+) - i(\infty)\} \times e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R_2}$$


Steady state Solution:

$$i(t \rightarrow \infty) = 0$$

$$i(t) = i(0^+) \times e^{-\frac{t}{\tau}}$$

Initial condition

Circuit for $t < 0$

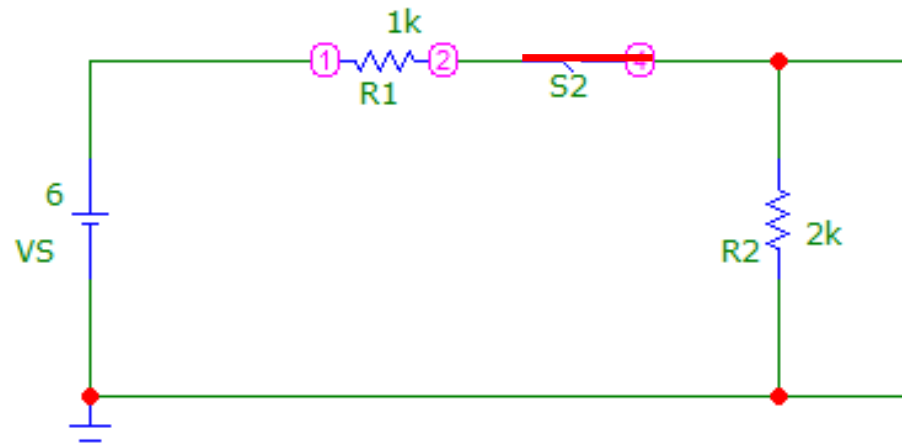


$$i(0^+) = i(0^-) = \frac{V_S}{R_1}$$



$$i(t \rightarrow \infty) = 0$$

$$i(t) = i(\infty) + \{i(0^+) - i(\infty)\} \times e^{-\frac{t}{\tau}}$$

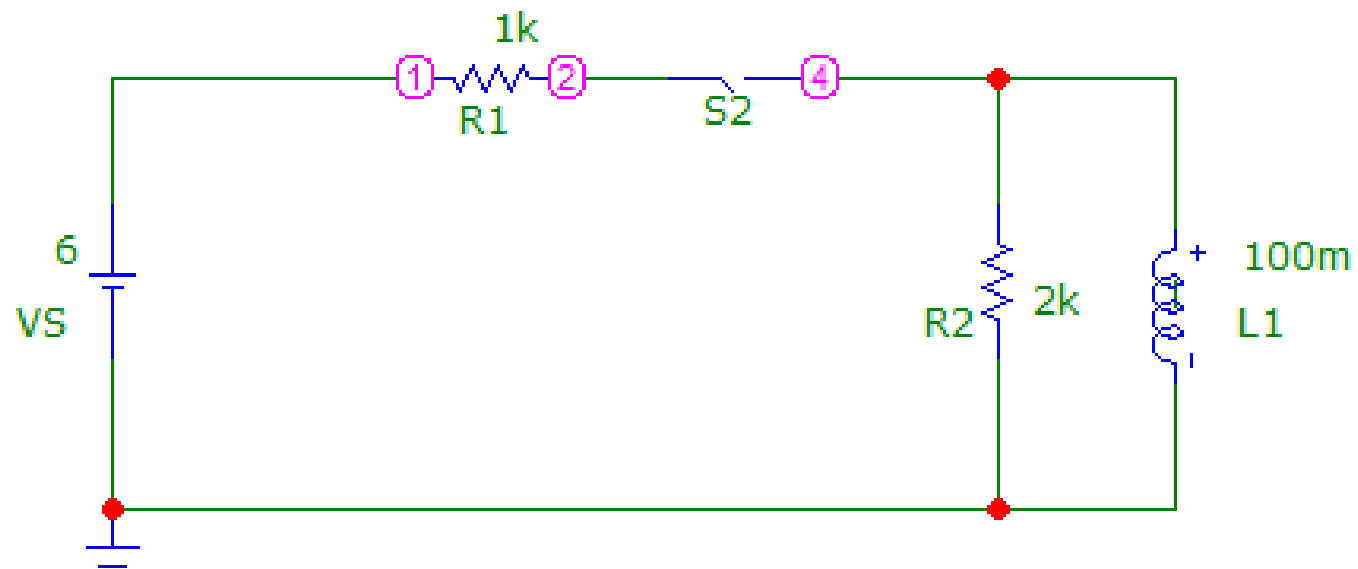
$$i(t) = \frac{V_S}{R_1} e^{-\frac{R_2}{L}t}$$


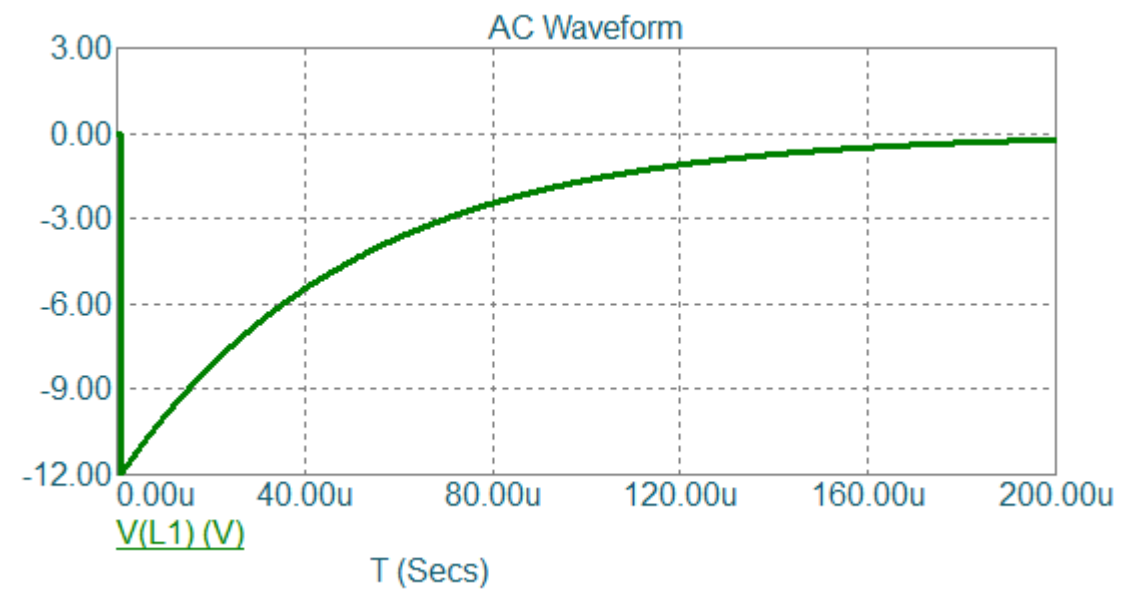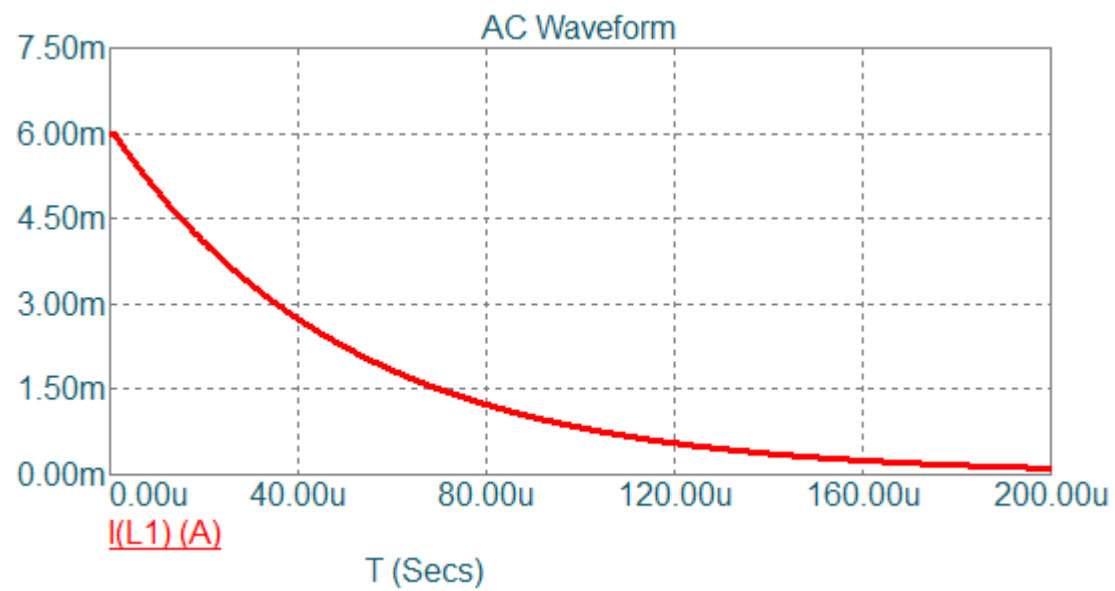
$$x(t) = x(\infty) + \{x(0^+) - x(\infty)\}e^{-\frac{t}{\tau}}$$



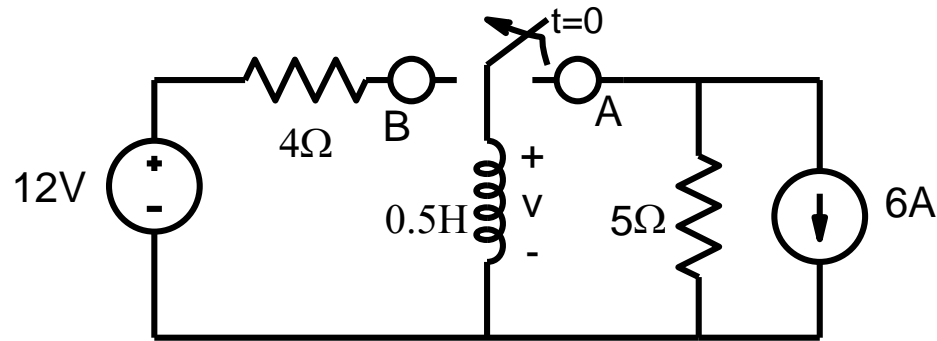Example: Determine the current and voltage across the inductor as a function of time after the switch is connected to node B.




$$i(t) = i(\infty) + \{i(0^+) - i(\infty)\} \times e^{-\frac{t}{\tau}}$$

Circuit after switch is connected to node B ($t > 0$)

$$\tau = \frac{L}{R_{eq}} = \frac{0.5}{4} = 0.125$$

$$i(\infty) = \frac{12}{4} = 3A$$

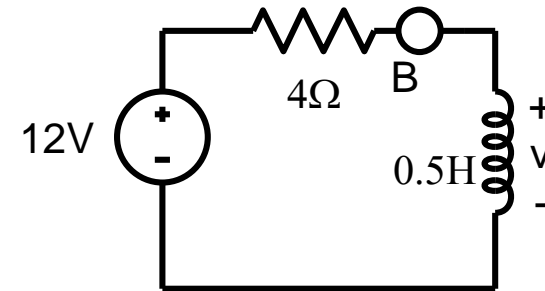




Next find current

$$i(0^+)$$

Inductor Current cannot change instantly

$$i(0^-) = i(0^+)$$

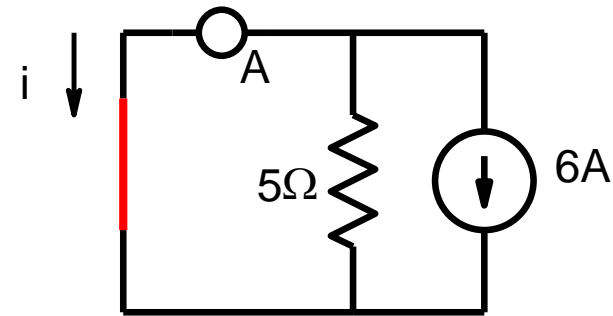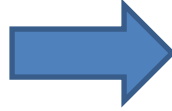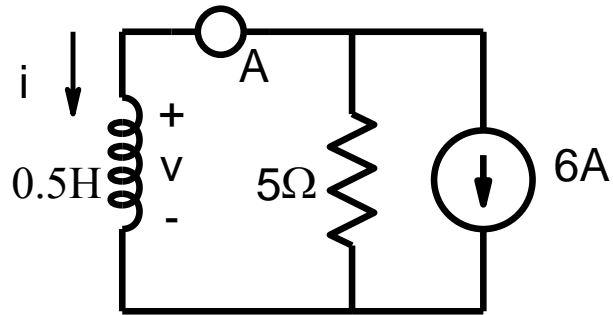Circuit before switch is connected to node B ($t < 0$)




$$i(0^-) = i(0^+) = -6A$$

$$i(t) = 3 - 9 \times e^{-8t}$$

$$v = L \frac{di}{dt} = 36 \times e^{-8t}$$

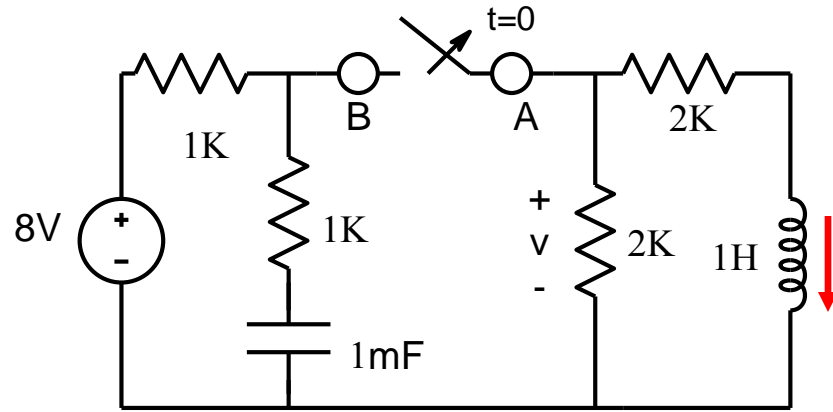Example: For the circuit shown below, determine the voltage v across the 2K resistor as a function of time after the switch is opened at $t=0$.




First find the inductor current

$$i_L(t) = i_L(\infty) + \{i_L(0^+) - i_L(\infty)\} \times e^{-\frac{t}{\tau}}$$

Circuit after opening the switch ($t > 0$)

$$R_{eq} = 2K + 2K = 4K$$

$$\tau = \frac{L}{R_{eq}} = 0.25ms$$

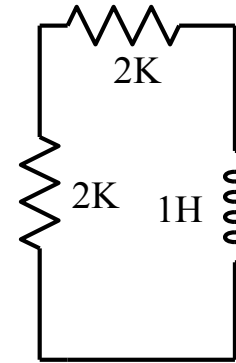


One can also see that :

$$i_L(\infty) = 0$$

$$i_L(0^+) = i_L(0^-)$$

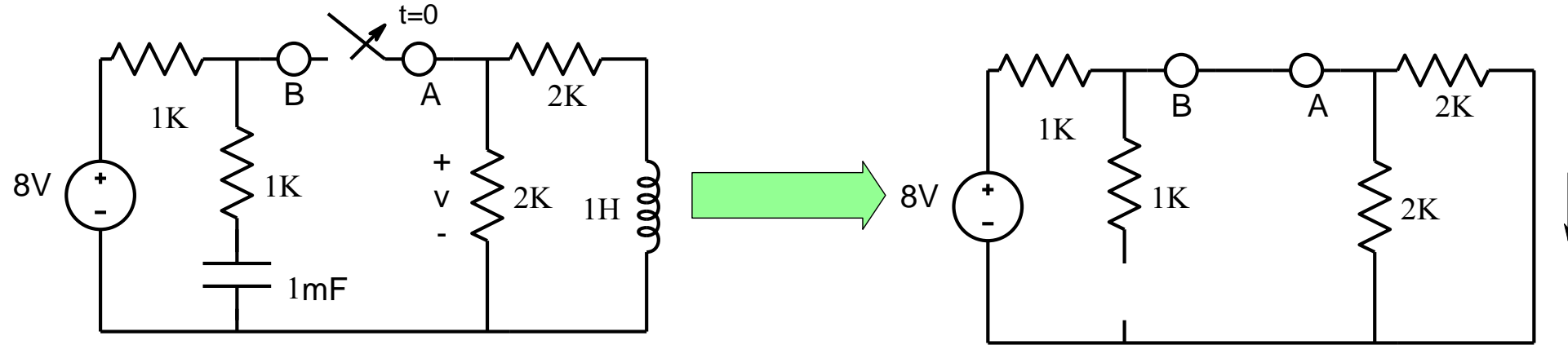
Circuit before opening the switch ($t < 0$) and assuming steady state condition:



$$i_L(0^+) = i_L(0^-) = \frac{8}{(2K \parallel 2K) + 1K} \times 0.5 = 2mA$$



$$\Rightarrow i_L(t) = 2 \times e^{-4000t} mA$$

Voltage across the 2K resistor:

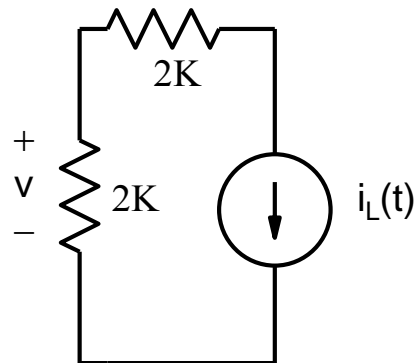


$$v(t) = -2 \times 10^3 \times i_L(t) = -4 \times e^{-4000t} V$$

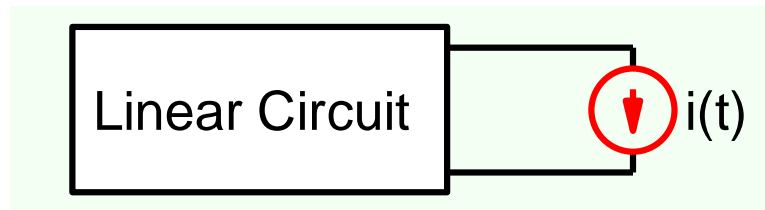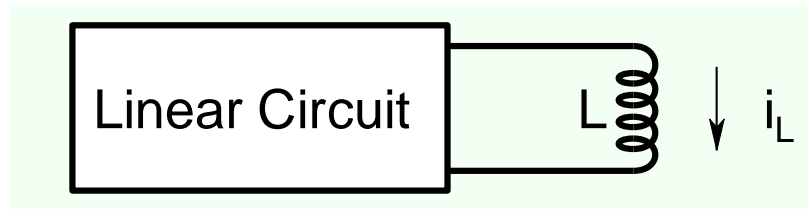How do we find voltages and currents elsewhere in the circuit?




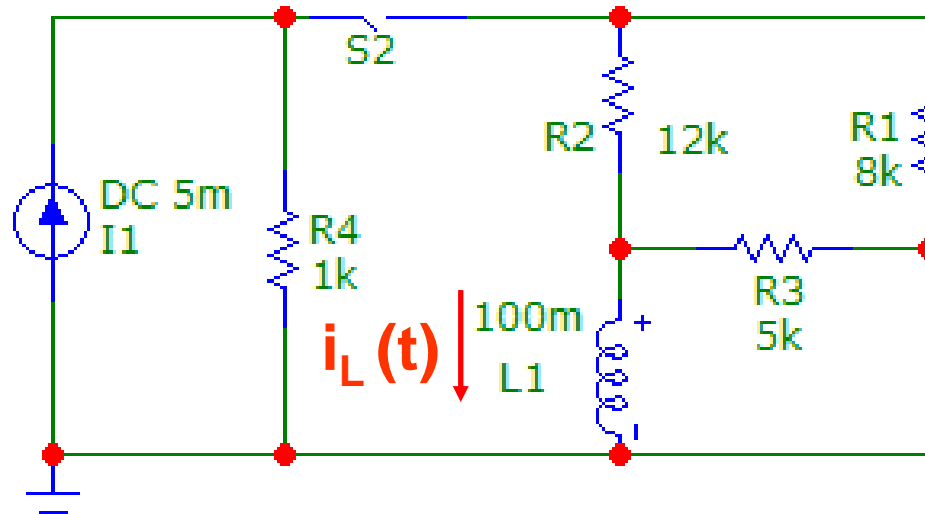Example:

Find current in 8 kΩ resistor as a function of time after the switch is opened


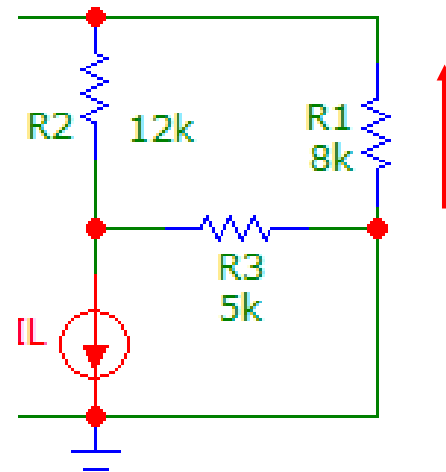
$$i_L(t) = 0.34mA \times e^{-\frac{t}{25\mu s}}$$



$$i_8 = i_L(t) \times \frac{5}{5 + 20} = 0.069mA \times e^{-\frac{t}{25\mu s}}$$